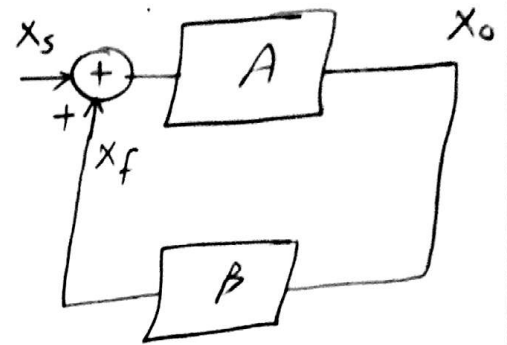


(1) In the fig. shown: the Frequency selective circuit exhibits a loss of -20 dB and phase shift of 180° .



What is the min. gain & phase shift that the amplifier must introduce for oscillations to start?

Solution

$$\beta|_{\text{dB}} = -20\text{ dB}$$

$$\beta|_{\text{dB}} = 20 \log(\beta) \Rightarrow \therefore -20 = 20 \log(\beta)$$

$$\therefore \beta = 0.1$$

\Rightarrow For osc. to start:


$$AB = 1$$

$$\therefore A(0.1) = 1$$

$$\therefore A = 10$$

(Actually: to start the osc., A must be greater than 10).

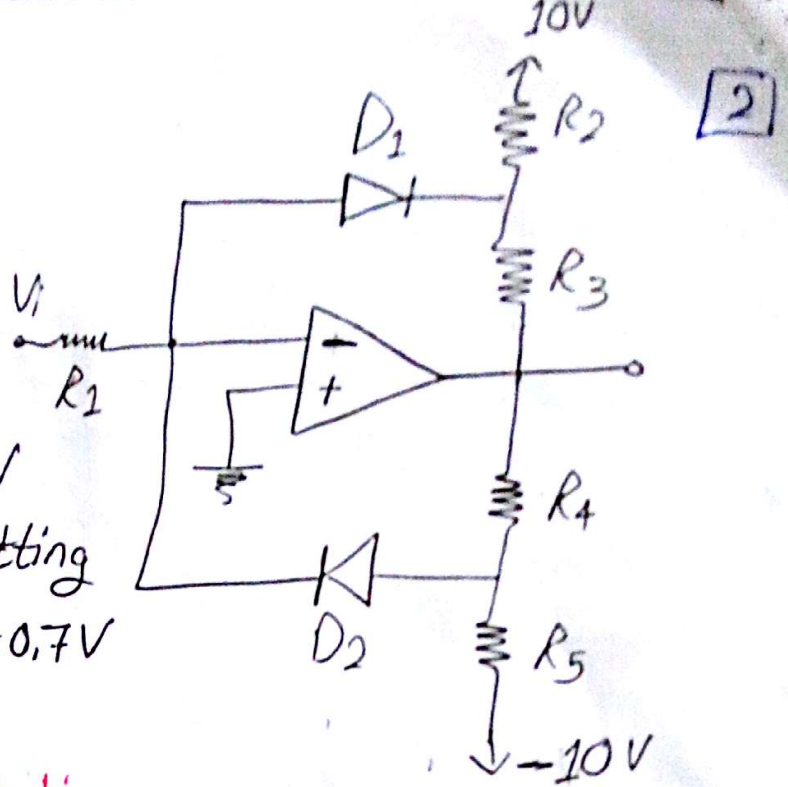(2) For the comparator circuit shown, Find suitable values for all resistors, so that the comparator levels are $\pm 6V$ and the slope of the limiting ch/s is -0.1 . Use $V_D = 0.7V$



Solution

⇒ The response of the comparator is:

Slope of the limiting region in general is:

$$\begin{aligned} &\rightarrow -\frac{R_3 \parallel R_f}{R_1} \text{ for } V_o \downarrow \\ &\rightarrow -\frac{R_4 \parallel R_f}{R_1} \text{ for } V_o \uparrow \end{aligned}$$

But $R_f = \infty$

$$\therefore \text{Slope} = -\frac{R_3}{R_1} = -\frac{R_4}{R_1} = 0.1 \rightarrow \textcircled{1}$$

$$\therefore R_3 = R_4 = 0.1 R_1$$

$$\Rightarrow L_+ = V \left(\frac{R_4}{R_5} \right) + V_D \left(1 + \frac{R_4}{R_5} \right)$$

$$\therefore 6 = 10 \left(\frac{R_4}{R_5} \right) + 0.7 \left(1 + \frac{R_4}{R_5} \right)$$

$$\therefore \frac{R_4}{R_5} = 0.4953 \rightarrow \textcircled{2}$$

$$\Rightarrow L_- = -V \left(\frac{R_3}{R_2} \right) - V_D \left(1 + \frac{R_3}{R_2} \right)$$

$$\therefore -6 = -10 * \frac{R_3}{R_2} - 0.7 \left(1 + \frac{R_3}{R_2} \right)$$

$$\therefore \frac{R_3}{R_2} = 0.4953 \rightarrow \textcircled{3}$$


\Rightarrow From $\textcircled{2}$ & $\textcircled{3}$:

$$\frac{R_3}{R_2} = \frac{R_4}{R_5} = 0.4953$$

But From $\textcircled{1}$: $R_3 = R_4 = 0.1 R_1 \checkmark$

$$\therefore R_2 = R_5 = \frac{0.1}{0.4953} R_1 \checkmark$$

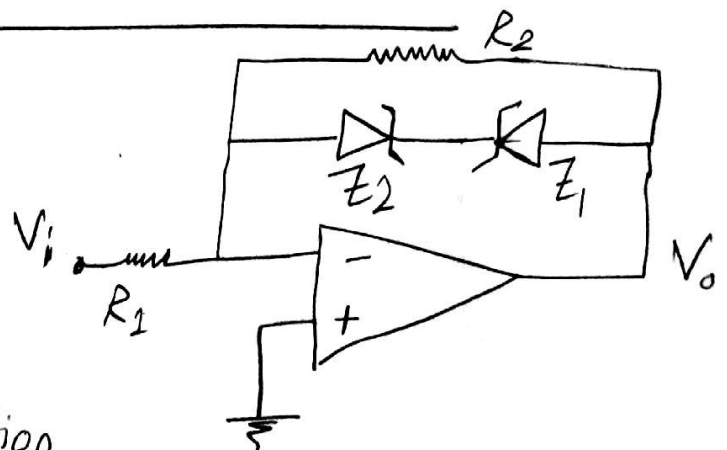(3) a) Sketch $V_o - V_i$
Characteristic
Curve



Solution

\Rightarrow When $V_i \downarrow \Rightarrow V_o \downarrow$

\therefore ~~Z~~ Z_1 & Z_2 are off

$$\therefore \frac{V_o}{V_i} = - \frac{R_2}{R_1}$$

\Rightarrow As $V_i \uparrow (+ve) \Rightarrow V_o \downarrow$ (more negative)

4

As V_o continues to decrease until it reaches the level $-(V_{Z_1} + V_{D_2})$

$\therefore Z_1$ & Z_2 are on


$$\therefore V_o = -(V_{Z_1} + V_{D_2})$$

$\Rightarrow V_i \downarrow$ (more negative) $\Rightarrow V_o \uparrow$ (+ve)

V_o continues to increase till it reaches $(V_{D_1} + V_{Z_2})$

$$\therefore V_o = V_{D_1} + V_{Z_2}$$

\therefore The Ch/s:

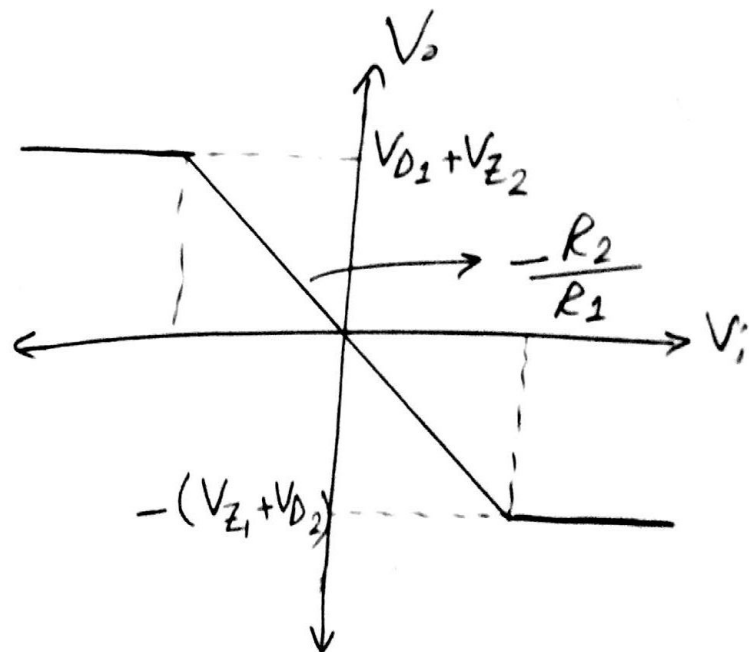

→ Repeated & Solved.

6


(4) The three circuits of limiting circuits that were demonstrated previously.

(5) Given the circuit shown. V_i $5nf$ $2k\Omega$ V_o
Draw the lead-lag response

Solution

$$f_r = \frac{1}{2\pi RC} = 15.92 kHz$$

↳ نقطة في المحاضرة

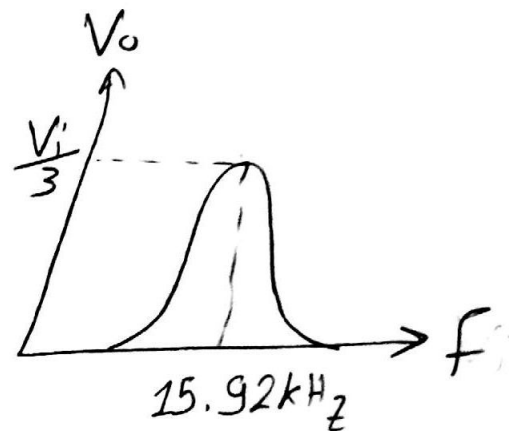

(6) a) Find the setting of potentiometer P at which osc. starts.

b) Find osc. frequency.

Solution


a) For osc. : $A\beta = 1$

$$\therefore \beta = \frac{1}{3} \Rightarrow A = 3$$

$$A = 1 + \frac{R_2 + R_p}{R_1} = 1 + \frac{10 + R_p}{50 - R_p}$$

$$\therefore 3 = 1 + \frac{10 + R_p}{50 - R_p}$$

$$\therefore R_p = 30k\Omega$$

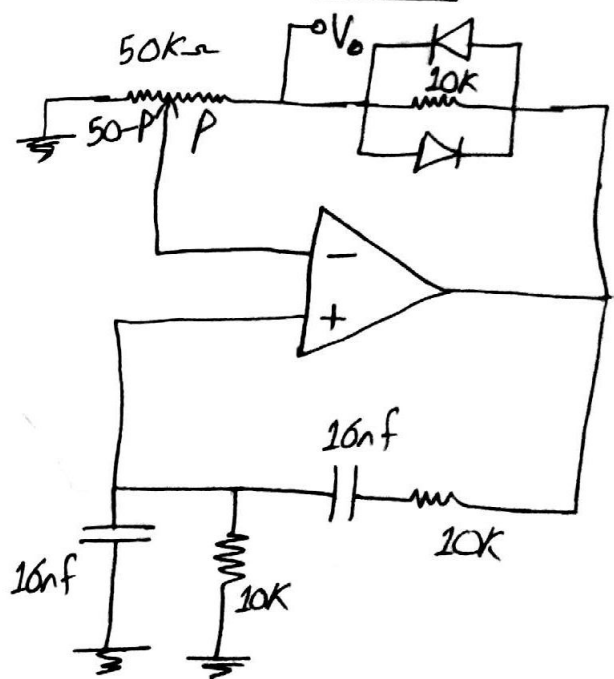

$$b) f_r = \frac{1}{2\pi RC} = 994.7 Hz$$

Find $V_{O_{P-P}}$

* Consider the +ve cycle of V_o .

$$\therefore \frac{V_o - V_D}{18} = \frac{V_b}{10}$$

$$\therefore \frac{1}{18} V_o = \left(\frac{1}{18} + \frac{1}{10} \right) V_o$$

But $V_D = \frac{V_a}{3}$

$$\therefore V_o = \frac{2.8}{3} V_a$$

$$\therefore V_0 = 0.933 V_a \rightarrow (1)$$


$$\Rightarrow I = I_1 + I_2$$

$$\therefore \frac{V_b}{10k} = \frac{V_a - V_o}{10k} + \frac{V_a - 0.7 - V_o}{0.1k}$$

$$\frac{V_b}{10 \times 10^3} = \frac{V_a}{10 \times 10^3} - \frac{V_o}{10 \times 10^3} + \frac{V_a}{100} - \frac{0,7}{100} - \frac{V_o}{100}$$

$$\therefore (10.1 \times 10^{-3}) V_a - 9.9 \times 10^{-3} \underbrace{V_o}_{0.933 \times V_b} - 7 \times 10^{-3} = 0.1 \times 10^{-3} \underbrace{V_b}_{\frac{V_a}{3}}$$
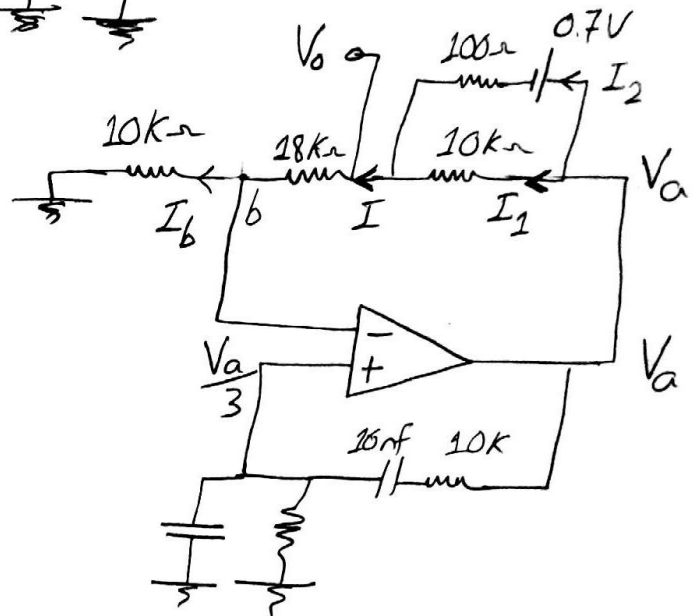
$$10.1 \times 10^{-3} \text{ V} \Rightarrow V_0 = 7.81 \text{ V} \Rightarrow V_{op-p} = 15.74 \text{ V}$$



(8) For the circuits shown:

- Check that oscillations start.
- Find the frequency of oscillation.
- Find the amplitude of the output sinusoid.

① a) $\beta = \frac{1}{3}$

$$A = 1 + \frac{R_f}{R_1} = 1 + \frac{40 + 20}{20}$$


$$\therefore A = 4$$

$$\therefore AB > 1$$

\therefore Oscillations will start.

b) $f_r = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 10 \times 10^3 \times 10 \times 10^{-9}}$

$$\therefore f_r = 1.591 \text{ kHz}$$

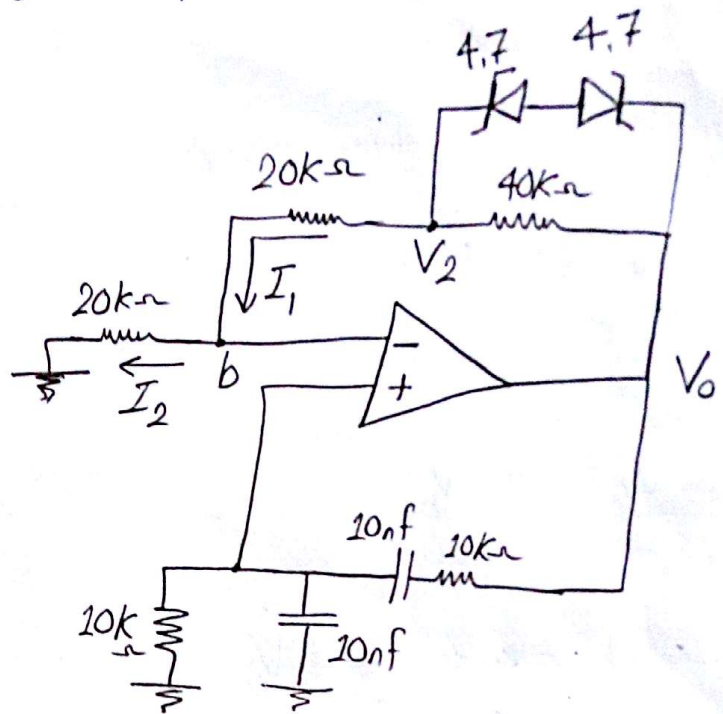

c) Consider the +ve cycle of V_0 :

$$V_2 = V_0 - (4.7 + 0.7) = V_0 - 5.4 \rightarrow \textcircled{1}$$

$$I_1 = I_2$$

$$\therefore \frac{V_2 - V_0}{20 \times 10^3} = \frac{V_0}{20 \times 10^3} \Rightarrow \frac{V_2}{20 \times 10^3} = \frac{V_0}{10 \times 10^3} \Rightarrow V_2 = 2V_0$$

$$\text{But } V_0 = \frac{V_0}{3}$$

$$\therefore V_2 = \frac{2}{3} V_0$$

From $\textcircled{1}$:

$$V_0 - 5.4 = \frac{2}{3} V_0$$

$$\therefore V_0 = 16.2 \text{ V}$$

③ a) $\beta = \frac{-1}{2g}$

$$A = -\frac{R_f}{R_1}$$

$$\therefore A = -\frac{20 + 20}{1}$$

$$A = -40$$

$$\therefore AB > 1$$

\therefore Oscillations start

$$b) f_r = \frac{1}{2\pi\sqrt{8RC}} = 64.97 \text{ kHz}$$

Phase Shift Oscillator

c) Consider +ve cycle of V_o :

$$D_2 \rightarrow \text{ON} \rightarrow 0.7V$$

$$V_b = -V \frac{1k}{1k+3k} + V_o \frac{3k}{3k+1k}$$

But $V_b = 0.7V \rightarrow$ في الشرح يتأكد

$$\therefore 0.7 = -10 \times \frac{1}{4} + V_o \times \frac{3}{4}$$

$$\therefore V_o = 4.27V$$

$$\therefore V_{o,p-p} = 8.59V$$

